



ELEC0020
Photonics Laboratory
Full Report

Suizhong Qin
Student ID: 17018962
Module Tutor: Dr Martyn Fice

Department: Electronic and Electrical Engineering
University College London

June 22, 2020

Abstract

This full lab report focuses on a simple photonics system and its essential characteristics. The LED or laser is used as the optical transmitter, and the photodiode is used as the optical receiver. An optical fibre connects these two major parts. Five laboratory tasks are required to conduct.

Record the data and plot the VI and LI diagrams for both LED and laser. The frequency response and square wave graphs are plotted to illustrate frequency response to a modulated laser. The attenuation of the POF is found by calculation. Eventually, observe the changes when the receiver load resistor is switched to the transimpedance receiver circuit.

Through the experiment, most measurement and calculated values are different from the typical values of the datasheet. Some of the uncertainties are inevitable, such as temperature. By analysing those recorded values, most errors are within an acceptable range.

Contents

1	Introduction	1
2	Preparation	1
3	Tasks	2
3.1	Task 1: Measure the Characteristics of the LED	2
3.1.1	Procedure	2
3.1.2	Result	3
3.1.3	Discussion	3
3.2	Task 2: Measure the Characteristics of the Laser Diode	3
3.2.1	Procedure	3
3.2.2	Result	4
3.2.3	Discussion	4
3.3	Task 3: Modulation of the Laser Diode and Frequency Response of System .	4
3.3.1	Procedure	4
3.3.2	Result	5
3.3.3	Discussion	6
3.4	Task 4: Measure the Loss of the Fibre	6
3.4.1	Procedure	6
3.4.2	Result and Discussion	6
3.5	Task 5: Transimpedance Amplifier	6
3.5.1	Procedure	6
3.5.2	Result and Discussion	7
4	Conclusion	7
	References	8
A	Lab Data Table	9
A.1	Task One	9
A.2	Task Two	10
A.3	Task Three	11

1 Introduction

Light can be seen everywhere in our daily life. The study involving light regards as photonics. By the discovery of properties of light, scientists found that photons are elementary particles of light, and light have wave-particle duality. Photonics is a vast and flourishing industry nowadays. Along with the development of this technology, the possibilities of photonics applications are limitless. For instance, solid-state lighting and optical communication[1]. Those applications bring high efficient lighting and communication systems.

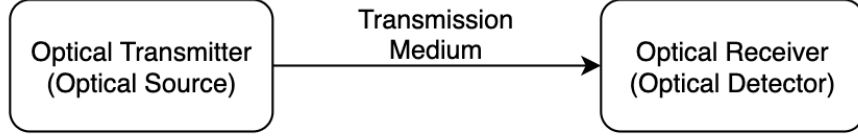


Figure 1: The General Photonics System

Figure 1 demonstrates the general form of the photonics system. There are three major parts in the system, optical transmitter, transmission medium, and optical receiver. As for the optical source, such as LED or laser, which produces modulated light from input signals. Then, the light propagates through the transmission medium, such as vacuum or optical fibre. Eventually, the optical detector receives the light[2]. The whole process makes up a simple photonics system.

This laboratory session aims for investigating the optical and electronic properties of some critical photonic components: an LED, a laser, and a photodiode(PD). The experiment conducts under a simple optical fibre communications system. Taking LED or laser as transmitter and photodiode as receiver, connecting two parts by an optical fibre. Besides, obtaining the optical fibre's attenuation value while the light propagates through the fibre.

2 Preparation

Before the experiment, an LED, a laser diode, and a photodiode are provided. From the datasheet of the LED and the laser diode, the part number for the LED is L-7113SRD-J4[3], which is a super bright red LED, and the part number for the laser diode is ADL-65055TL[4]. Both the LED and the laser diode use AlGaInP as the semiconductor material. The **dominant emission wavelength** for the LED is around **640nm**, and the typical wavelength for the laser is around **655 nm**. As for the **spectral width**, the LED has **40nm** and the laser has **15nm**. The typical threshold current for the laser is 18mA at 25 °C. From the datasheet, the I_{th} is about 23.5mA at 50 °C. The equation for the characteristic temperature T_0 is:

$$\frac{I_{th}(T_1)}{I_{th}(T_2)} = \exp \left[\frac{(T_1 - T_2)}{T_0} \right] \quad (2.1)$$

Therefore, the T_0 is approximately 93.8K.

From the graph in the LED datasheet, the forward voltage is around $2.13V$ when the forward current is $25mA$. The resistance of the series resistor should be: $R = \frac{V_S - V_F}{I_F} = \frac{5V - 2.13V}{25mA} = 114.8\Omega$. As for the laser diode, the I-V graph shows the voltage is about $2.15V$ when the operating current is $25mA$. Thus, for the laser diode: $R = \frac{V_S - V_F}{I_F} = \frac{5V - 2.15V}{25mA} = 114\Omega$. These two values are quite similar.

For the last essential components, the photodiode, which the part number is BPW20RF[5]. Silicon PN junction is the semiconductor material to fabricate this photodiode. Under the spectral range between $400nm$ and $1100nm$, the photodiode can perform normally. The absolute maximum reverse voltage is $10V$, and the capacitance is around $400pF$ when $V_R = 5V$. Since the typical operating current for the laser diode is $25mA$, and $P_0 = 5mW$. The value for the photodiode responsivity is: $R_s = \frac{I_0}{P_0} = 0.38A/W$. Before the experiment, laser safety is a critical topic. Since the laser used in the lab is Class 2 laser, the plastic cover of the laser should not be removed at any time during the experiment.

3 Tasks

3.1 Task 1: Measure the Characteristics of the LED

3.1.1 Procedure

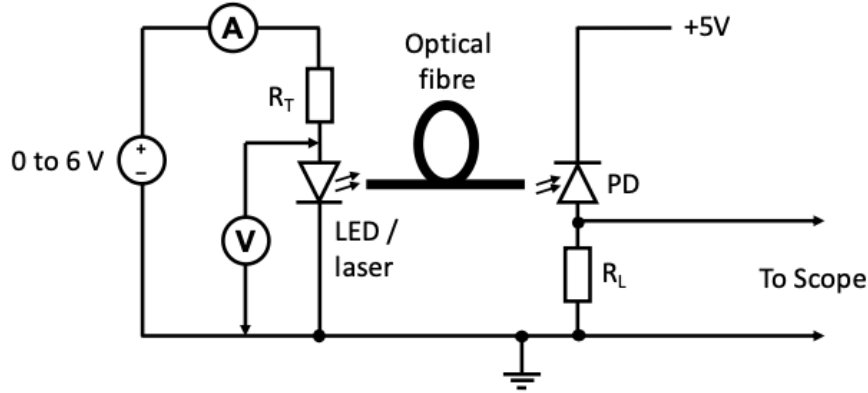


Figure 2: The Circuit Diagram for LED or Laser Photonics System[6]

Figure 2 illustrates the circuit diagram of LED or laser photonics system. In this task, the LED is used as optical transmitter, and photodiode as optical receiver. Connecting two major parts by a one meter optical fibre. The power supply sets to $5V$ DC. In order to ensure the forward current is $25mA$, the forward voltage should be approximately $2.13V$. This value comes from the graph in the LED datasheet. Hence, the resistance of R_T should be $R_T = \frac{V_S - V_F}{I_F} = \frac{5V - 2.13V}{25mA} = 114.8\Omega$, which is stated in the Preparation section.

To ensure the safety of the circuit, setting the LED power supply current and voltage limits to $30mA$ and $6V$ respectively. Setting the photodiode power supply current and voltage limits

to $5mA$ and $6V$ respectively. The LED should be forward-bias and the photodiode should be reverse-bias. After building the entire circuit, varying the LED's forward current in a range up to $25mA$. Recording voltage values across the LED and photodiode's load resistor. Later, using the recording data to plot VI(voltage-current) and LI(light-current) diagrams.

3.1.2 Result

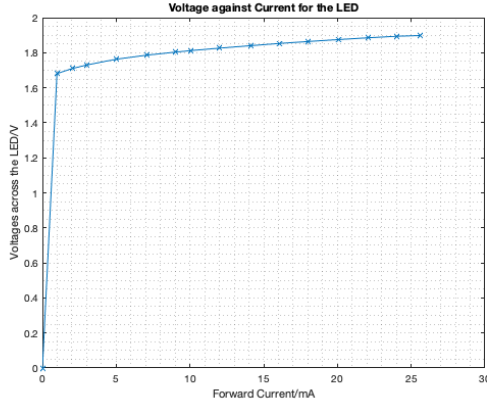


Figure 3: V-I Diagram for the LED

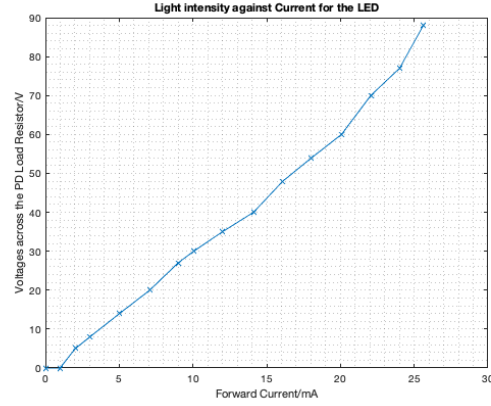


Figure 4: L-I Diagram for the LED

In Appendix A.1, Table 1 demonstrates the lab data. The data is plotted in Figure 3 and 4. From the Figure 3, when the forward current is $25mA$, the voltage across the LED is around $1.895V$. As for the Figure 4, it shows light intensity against forward current. When the LED forward current is $25mA$, the light intensity is around $87mV$. According to the formula and obtaining the current in the PD circuit: $I = \frac{87mV}{10k\Omega} = 8.7 \times 10^{-6}A$, and the optical power is: $P = \frac{I_0}{R} = \frac{8.7 \times 10^{-6}A}{0.38A/W} = 2.29 \times 10^{-5}W$.

3.1.3 Discussion

The pattern for the Figure 3 is typical. The forward voltage is $1.895V$ when the forward current is $25mA$. By comparing it with the datasheet value, around $2.12V$, they are slightly different. The shape for Figure 4 is sub-linear; this is due to the internal quantum efficiency is lower at a higher temperature. The final optical power detected by the PD is approximately $2.29 \times 10^{-5}W$; this value is lower than the ideal value. Since the optical fibre connectors in our group are too loose, some energy dissipates at both ends of the optical fibre.

3.2 Task 2: Measure the Characteristics of the Laser Diode

3.2.1 Procedure

In this task, the general circuit is unchanged, and replacing the LED with the laser diode. It is aimed to investigate the characteristics of the laser diode. From the previous calculation, the resistance of the series resistor is: $R_T = 114\Omega$, which means the series resistor R_T does not need to change. Then, repeating the same procedures as the Task one. Recording the values of voltage across the laser and the PD's load resistor.

3.2.2 Result

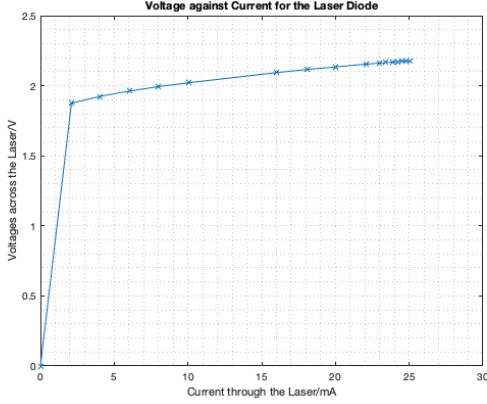


Figure 5: V-I Diagram for the Laser

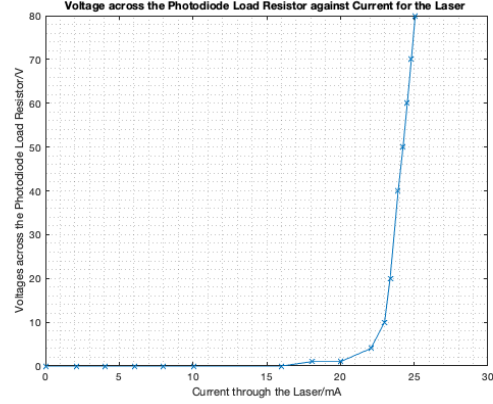


Figure 6: Voltage across PD's Load Resistor against I Diagram for the Laser

In Appendix A.2, Table 2 shows the recorded data from task two. The data is plotted in Figure 5 and 6. From Figure 6, the threshold current is about $20mA$. By comparing it with the value from the laser datasheet, a typical threshold current is about $18mA$.

3.2.3 Discussion

By comparison, Figure 3 and 5 have similar patterns. From Figure 5, the operating voltage is about $2.2V$, which is higher than the forward voltage of the LED. From the datasheet, the typical operating voltage is $2.2V$, which matches the real measurement result. As for the Figure 4 and 6, they have different shapes. Figures 6 can identify the threshold current, which is about $20mA$. Due to some external conditions, such as temperature. The real threshold current is higher than the ideal one.

3.3 Task 3: Modulation of the Laser Diode and Frequency Response of System

3.3.1 Procedure

Keeping the basic circuit unchanged, removing the current-meter and the volt-meter from the circuit. Changing the power supply to the AC source. The Task 3 is aimed for investigation of laser diode modulation and the frequency response of this system. Before the modulation, biasing the laser above the threshold current with a DC offset is necessary. The biased laser current should be the halfway between the threshold current and $25mA$.

$$I_{bias} = \frac{I_{th} + 25mA}{2} = 22.5mA \quad (3.2)$$

Thus, the DC offset voltage can be deduced: $V_{offset} = (R_T + R_{in}) \times I + V_{operating} = (114\Omega + 50\Omega) \times 0.0225A + 2.2V = 5.89V$. Then, vary the peak-to-peak current from I_{th} to $25mA$,

and determine the peak-to-peak voltage as well. To ensure the safety of the circuit, the maximum current should not exceeds $25mA$. The peak-to-peak voltage is:

$$V_{pp} = (25mA - I_{th}) \times (R_{in} + R_T) = 0.82V \quad (3.3)$$

After the calculation, setting the signal generator to $1kHz$ sine wave and DC offset, $V_{offset} = 5.89V$, and the $V_{pp} = 0.82V$. Then, adjusting the bias voltage and V_{pp} until getting a clear and undistorted sine wave without exceeding the $25mA$. Varying the frequency, and record the receiver voltage, which is the output voltage. Therefore, the graph of frequency response against frequency can be plotted. Later, use the same signal generator settings to produce a square wave. Record the extinction ratio of the received signal at $1kHz$. Finally, observe patterns from the oscilloscope when frequencies rise.

3.3.2 Result

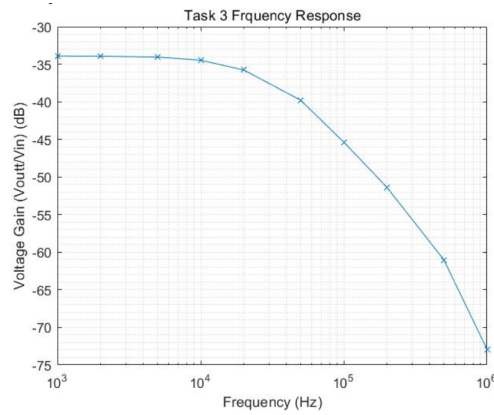


Figure 7: The Frequency Response against Frequency

When the frequency response is $-3dB$, the bandwidth is around $30kHz$. The equation for the bandwidth is: $f_c = \frac{1}{2\pi R_L C} = \frac{1}{2\pi \times 10k\Omega \times 400pF} = 3.98kHz$. Thus, the expected bandwidth should be $3.98kHz$.

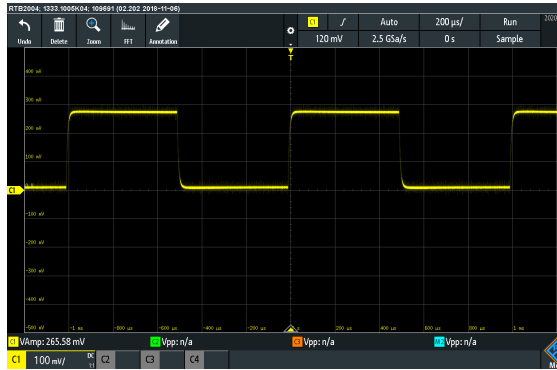


Figure 8: The Square Wave for 1kHz Frequency

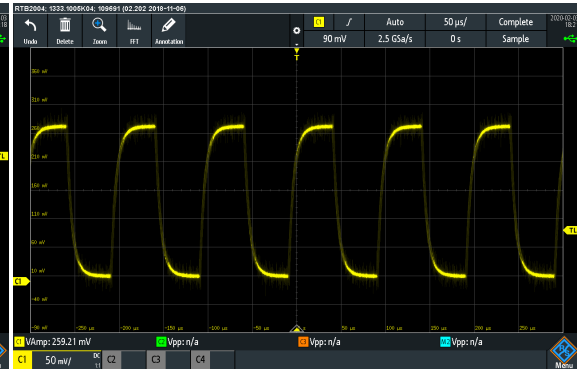


Figure 9: The Square Wave for 10kHz Frequency

3.3.3 Discussion

From the equation $f_c = \frac{1}{2\pi R_L C}$, the main factor to determine the bandwidth is the capacitance of the photodiode. By calculation, the $f_c = 3.98kHz$, which is smaller than the value on the datasheet. Since the reverse voltage is less than 5V for the PD circuit, and the capacitance is greater than the value from the datasheet. Overall, the real value is smaller than the ideal one. When the PD reverse bias is changed from 0V to 5V, the depletion zone will rise, which means the PD's capacitance will fall. From the previous equation, the f_c will increase. This will result a rise in bandwidth.

3.4 Task 4: Measure the Loss of the Fibre

3.4.1 Procedure

This task is aimed for measuring the loss of the optical fibre. Firstly, there is an equation to estimate whether a fibre is single-mode or multi-mode:

$$V = \frac{2\pi a}{\lambda} \times \text{NumericalAperture} \quad (3.4)$$

In this equation, a is the radius of the fibre, and it is 0.5mm for this fibre. The λ is the wavelength in vacuum. The numerical aperture is 0.47. The boundary to decide whether it is single-mode or multi-mode is 2.405. Any values above 2.405 consider as single-mode. In this task, the value is higher than 2.405. Therefore, the fibre is single-mode. Then, use the same circuit in Task 3, and modulate the laser with a 1kHz sine wave. Adjust the offset and V_{pp} to get a clear and undistorted diagram. A new ten meter fibre is provided, use this fibre connects with the one meter fibre, and repeat the same procedure as the previous measurement.

3.4.2 Result and Discussion

Set the V_{pp} to 850mV, and the amplitude of the received signal is 136.78mV. When two fibres are connected together, the total length is 11 meter, and the amplitude of the received signal is 25.67mV, which is much smaller than the previous value. The equation for the attenuation of the POF is :

$$\alpha_{dB} = -20 \frac{1}{L} \log_{10} \frac{V_{new}}{V_{old}} \quad (3.5)$$

The attenuation of the POF is therefore about 1.45 dB/m

3.5 Task 5: Transimpedance Amplifier

3.5.1 Procedure

Use a simple circuit of the transimpedance receiver. The operational amplifier made by ZX-741. This circuit is used to substitute the original load resistor receiver. Ensure the $R_f = R_L$ to obtain the same output voltage. Drive the laser by the method in task 3, generating the square wave and observe the output voltage. Then, add another compensation capacitor parallel to the R_f and observe the output voltage.

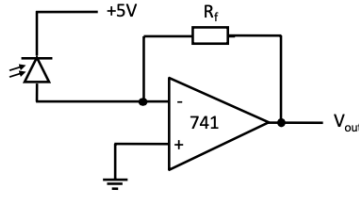


Figure 10: Transimpedance Receiver Circuit Diagram

3.5.2 Result and Discussion

When there is no compensation capacitor, the transient response is that the ringing on the signal at the upper and lower edges of the square wave, and amplitudes attenuate gradually. In a very short time, the signal becomes a horizontal line. By adding a $100pF$ compensation capacitor, there are fewer oscillations, and the graph becomes clear with less noise. Noise is produced while the light propagates through the fibre. The compensation capacitor is used as a low-pass filter to eliminate some noise.

4 Conclusion

By investigating different photonics components, such as LED, laser diode, and photodiode, and analysing recorded data during the experiment, a better understanding of the basic photonics system is developed. This report explores the characteristics of the LED and the laser, the frequency response when the laser is modulated, and the properties of optical fibre. Those are the base of a simple photonics system. Photonics is a growing industry, and it benefits human from all aspects of daily life.

References

- [1] Dr Martyn Fice. (n.d.). ELEC0020 Photonics and Communications Systems. p.Note for Lecture one, Page 5.
- [2] Dr Martyn Fice. (n.d.). ELEC0020 Photonics and Communications Systems. p.Note for Lecture one, Page 8.
- [3] Cui, F. (2012). LED Data Sheet. Kingbright, pp.Page 1, 2, 3.
- [4] AlGaInP Visible Laser Diode. (2020). 1st ed. LASER COMPONENTS IG, Inc., pp.Page 1, 2.
- [5] Silicon Photodiode, RoHS Compliant. (2011). 1st ed. Vishay Semiconductors, pp.Page 1, 2, 3.
- [6] Dr Martyn Fice. (2020). ELEC0020: Photonics and Communication Systems Photonics Laboratory. UCL Electronic and Electrical Engineering, p.Page 4.

A Lab Data Table

A.1 Task One

Table 1: Data from Task One

Forward Current/mA	Forward Voltage/V	Voltage across PD Load Resistor/mV
0.986	1.680	0
2.029	1.710	5
3.016	1.730	8
5.025	1.763	14
7.075	1.786	20
8.991	1.803	27
10.052	1.812	30
12.002	1.826	35
14.106	1.840	40
16.095	1.853	48
18.038	1.864	54
20.073	1.875	60
22.055	1.885	70
24.007	1.894	77
25.620	1.898	88

A.2 Task Two

Table 2: Data from Task Two

Laser Current/mA	Laser Voltage/V	Voltage across PD Load Resistor/mV
0	0	0
2.102	1.875	0
4.027	1.924	0
6.046	1.962	0
8.012	1.994	0
10.027	2.021	0
16.028	2.094	0
18.074	2.116	1
20.003	2.134	1
22.058	2.154	4
22.992	2.161	10
23.367	2.165	20
23.915	2.169	40
24.245	2.172	50
24.533	2.174	60
24.808	2.176	70
25.069	2.179	80

A.3 Task Three

Table 3: Data from Task Three

Vout/V	Vin/V	Frequency Response/dB	Frequency/kHz
0.2872	0.82	0.350243902	1
0.2872	0.82	0.350243902	2
0.2862	0.82	0.34902439	4
0.2832	0.82	0.345365854	6
0.2784	0.82	0.339512195	8
0.2714	0.82	0.33097561	10
0.2646	0.82	0.322682927	12
0.2577	0.82	0.314268293	14
0.2489	0.82	0.303536585	16
0.2413	0.82	0.294268293	18
0.2185	0.82	0.266463415	20
0.2131	0.82	0.259878049	22
0.2058	0.82	0.25097561	24
0.198	0.82	0.241463415	26
0.186	0.82	0.226829268	30
0.1685	0.82	0.205487805	35
0.1538	0.82	0.187560976	40
0.132	0.82	0.16097561	50
0.112	0.82	0.136585366	60
0.098	0.82	0.119512195	70
0.0863	0.82	0.105243902	80
0.0734	0.82	0.089512195	100